



Hacettepe University

ELE432 Advanced Digital Design

Experiment 1- ALU and FSM Design and Implementation

Mehmet Yücel Sarıtaş
21990451

Lecturer : Prof.Dr. Ali Ziya Alkar

Question 1)

Write a VHDL code that implements an ALU that does arithmetic operations (addition, subtraction, multiplication etc.) and logic operations (and, or, invert, xor etc.) with the use of 4 switches on the board

Implementation of ALU

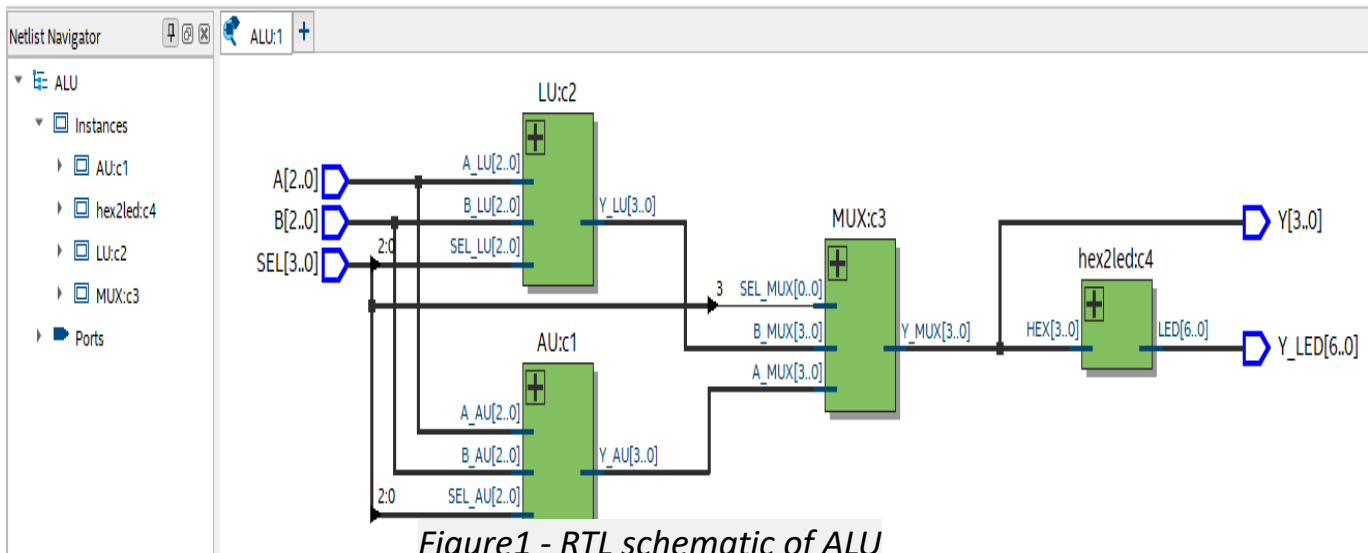


Figure1 - RTL schematic of ALU

Comment: In my design, I have used 3 components that make my ALU implementation more modular. These are as follows; AU (Arithmetic Unit), LU (Logic Unit), and Hex to seven-segment display converter. To see results in both binary and display formats I have outputted 2 signals one of them is Y[3..0] other one is Y_LED[6..0].

VHDL Code of Design

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;

entity ALU is
    port
    (
        A          : in unsigned (2 downto 0);
        B          : in unsigned (2 downto 0);
        SEL        : in unsigned (3 downto 0);
        Y          : out unsigned (3 downto 0);
        Y_LED      : out std_logic_vector (6 downto 0)
    );
end ALU;

architecture rtl of ALU is

    component AU is
        port
        (
            A_AU      : in unsigned (2 downto 0);
            B_AU      : in unsigned (2 downto 0);
            SEL_AU     : in unsigned (2 downto 0);
            Y_AU       : out unsigned (3 downto 0)
        );
    end component;

    component LU is
        port
        (
            A_LU      : in unsigned (2 downto 0);
            B_LU      : in unsigned (2 downto 0);
            SEL_LU     : in unsigned (2 downto 0);
            Y_LU       : out unsigned (3 downto 0)
        );
    end component;
```

Code1 - VHDL of ALU design

```

component MUX is
    port
    (
        A_MUX      : in unsigned (3 downto 0);
        B_MUX      : in unsigned (3 downto 0);
        SEL_MUX     : in unsigned (0 downto 0);
        Y_MUX       : out unsigned (3 downto 0)
    );
end component;

component hex2led is
    PORT (
        HEX : IN STD_LOGIC_VECTOR (3 DOWNTO 0);
        LED : OUT STD_LOGIC_VECTOR (6 DOWNTO 0)
    );
end component;

SIGNAL temp1: unsigned (3 downto 0);
SIGNAL temp2: unsigned (3 downto 0);
SIGNAL temp3: unsigned (3 downto 0);

begin
    c1: AU port map(A_AU => A, B_AU => B, SEL_AU => SEL(2 downto 0), Y_AU => temp1);
    c2: LU port map(A_LU => A, B_LU => B, SEL_LU => SEL(2 downto 0), Y_LU => temp2);
    c3: MUX port map(A_MUX => temp1, B_MUX => temp2, SEL_MUX => SEL(3 downto
3),Y_MUX => temp3);
    Y <= temp3;
    c4: hex2led port map(HEX => std_logic_vector(temp3), LED => Y_LED);
end rtl;
    
```

Code2 - VHDL of ALU design

VHDL Implementation of AU (Arithmetic Unit)

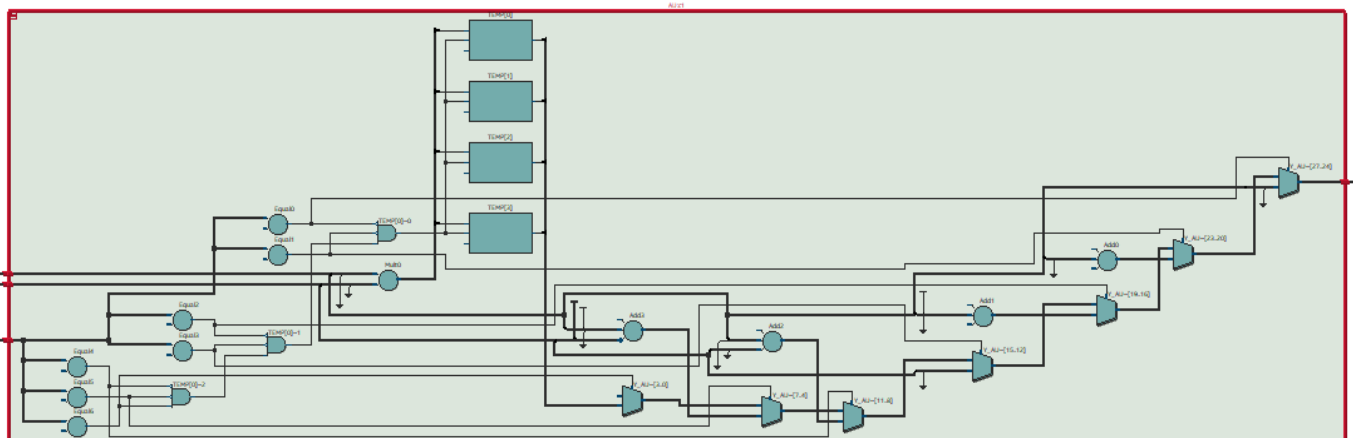


Figure2 - RTL schematic of AU

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;

entity AU is
    port
    (
        A_AU      : in unsigned (2 downto 0);
        B_AU      : in unsigned (2 downto 0);
        SEL_AU     : in unsigned (2 downto 0);
        Y_AU      : out unsigned (3 downto 0)
    );
end entity;

architecture rtl of AU is
    SIGNAL TEMP: unsigned (7 DOWNTO 0);
    SIGNAL A_TEMP: unsigned (3 DOWNTO 0);
    SIGNAL B_TEMP: unsigned (3 DOWNTO 0);
begin
    process(A_AU,B_AU,SEL_AU) --a,b,SEL are sensivity lists)
    begin
        A_TEMP <= "0" & A_AU;
        B_TEMP <= "0" & B_AU;
        -- add if "add_sub" is 1, else subtract
        if (SEL_AU = "000") then
            Y_AU <= A_TEMP;
        elsif (SEL_AU = "001") then
            Y_AU <= A_TEMP + 1;
        elsif (SEL_AU = "010") then
            Y_AU <= A_TEMP - 1;
        elsif (SEL_AU = "011") then
            Y_AU <= B_TEMP;
        elsif (SEL_AU = "100") then
            Y_AU <= A_TEMP + B_TEMP;
        elsif (SEL_AU = "101") then
            Y_AU <= A_TEMP - B_TEMP;
        elsif (SEL_AU = "110") then
            TEMP <= A_TEMP*B_TEMP;
            Y_AU <= TEMP(3 DOWNTO 0);
        else
            Y_AU <= "0000";
        end if;
    end process;
end rtl;
```

Code3 - VHDL of AU design

VHDL Implementation of LU (Logic Unit)

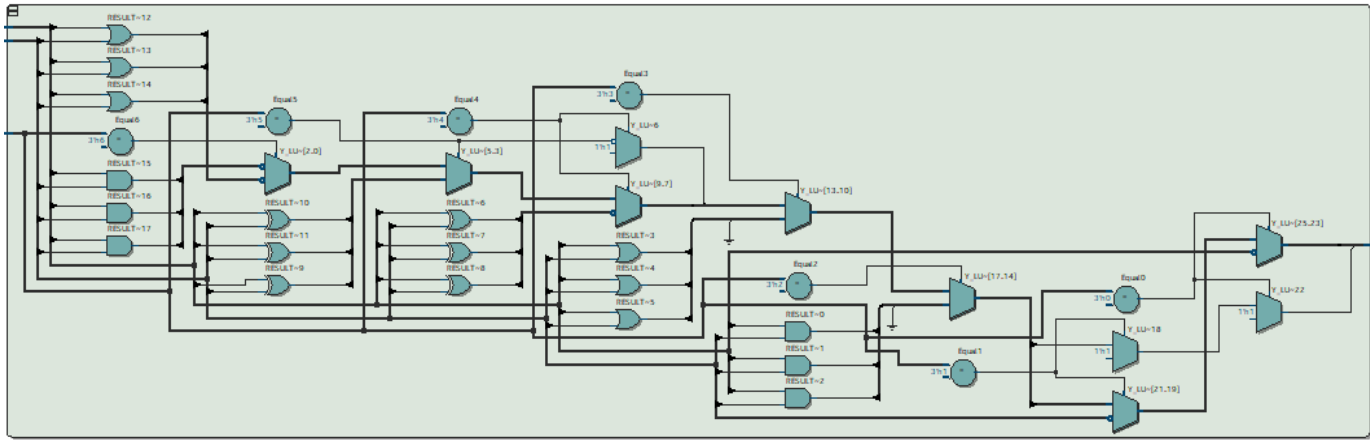


Figure3 - RTL schematic of LU

```

library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;

entity LU is
    port
    (
        A_LU      : in unsigned (2 downto 0);
        B_LU      : in unsigned (2 downto 0);
        SEL_LU    : in unsigned (2 downto 0);
        Y_LU      : out unsigned (3 downto 0)
    );
end entity;

architecture rtl of LU is
    SIGNAL TEMP: unsigned (7 DOWNTO 0);
    SIGNAL A_TEMP: unsigned (3 DOWNTO 0);
    SIGNAL B_TEMP: unsigned (3 DOWNTO 0);

begin

    process(A_LU,B_LU,SEL_LU) --a,b,SEL are sensivity lists(when one of
    them changed processes triggered)

```

Code4 - VHDL of LU design

```
begin
    A_TEMP <= "0" & A_LU;
    B_TEMP <= "0" & B_LU;
    -- add if "add_sub" is 1, else subtract
    if (SEL_LU = "000") then
        Y_LU <= NOT A_TEMP;
    elsif (SEL_LU = "001") then
        Y_LU <= NOT B_TEMP;
    elsif (SEL_LU = "010") then
        Y_LU <= A_TEMP AND B_TEMP;
    elsif (SEL_LU = "011") then
        Y_LU <= A_TEMP OR B_TEMP;
    elsif (SEL_LU = "100") then
        Y_LU <= A_TEMP XNOR B_TEMP;
    elsif (SEL_LU = "101") then
        Y_LU <= A_TEMP XOR B_TEMP;
    elsif (SEL_LU = "110") then
        Y_LU <= A_TEMP NOR B_TEMP;
    else
        Y_LU <= A_TEMP NAND B_TEMP;
    end if;
end process;
end rtl;
```

Code5 - VHDL of LU design

VHDL Implementation of MUX

 


Figure4 - RTL schematic of MUX

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;

entity MUX is

    port
    (
        A_MUX          : in unsigned (3 downto 0);
        B_MUX          : in unsigned (3 downto 0);
        SEL_MUX        : in unsigned (0 downto 0);
        Y_MUX          : out unsigned (3 downto 0)
    );

end entity;

architecture rtl of MUX is

begin

    process(A_MUX,B_MUX,SEL_MUX) --a,b,SEL are sensitivity
lists(when one of them changed processes triggered)

    begin

        if (SEL_MUX = "0") then
            Y_MUX <= A_MUX;
        else
            Y_MUX <= B_MUX;
        end if;

    end process;

end rtl;
```

Code6 - VHDL of MUX design



Simulation Results of ALU

A AND B (A = 110, B=001, SEL = 1010)

Name	Value at 0 ps	0 ps	80,0 ns	160,0 ns	240,0 ns	320,0 ns	400,0 ns	480,0 ns	560,0 ns	640,0 ns	720,0 ns	800,0 ns	880,0 ns	960,0 ns
▶ A	B 110							110						
▶ B	B 001							001						
▶ SEL	B 1010							1010						
▶ Y	B 0000							0000						
▶ Y_LED	B 1000000							1000000						

Simulation1- A and B

A * B (A = 110, B=001, SEL = 0110)

Name	Value at 0 ps	0 ps	80,0 ns	160,0 ns	240,0 ns	320,0 ns	400,0 ns	480,0 ns	560,0 ns	640,0 ns	720,0 ns	800,0 ns	880,0 ns	960,0 ns
▶ A	B 110							110						
▶ B	B 001							001						
▶ SEL	B 0110							0110						
▶ Y	B 0110							0110						
▶ Y_LED	B 0000010							0000010						

Simulation2- A * B

A + B (A = 110, B=001, SEL = 0100)

Name	Value at 0 ps	0 ps	80,0 ns	160,0 ns	240,0 ns	320,0 ns	400,0 ns	480,0 ns	560,0 ns	640,0 ns	720,0 ns	800,0 ns	880,0 ns	960,0 ns
▶ A	B 110							110						
▶ B	B 001							001						
▶ SEL	B 0100							0100						
▶ Y	B 0111							0111						
▶ Y_LED	B 1111000							1111000						

Simulation3- A + B

A XOR B (A = 110, B=001, SEL = 0100)

Name	Value at 0 ps	0 ps	80,0 ns	160,0 ns	240,0 ns	320,0 ns	400,0 ns	480,0 ns	560,0 ns	640,0 ns	720,0 ns	800,0 ns	880,0 ns	960,0 ns
▶ A	B 110							110						
▶ B	B 001							001						
▶ SEL	B 1101							1101						
▶ Y	B 0111							0111						
▶ Y_LED	B 1111000							1111000						

Simulation4- A xor B



Pin Planner of ALU Design

All Pins								
Named: <input type="text"/> Edit: <input type="button" value="X"/> <input type="button" value="✓"/>								
Node Name	Direction	Location	I/O Bank	VREF Group	I/O Standard	Reserved	Current Strength	Slew Rate
in A[2]	Input	PIN_AD12	3A	B3A_N0	2.5 V (default)		12mA (default)	
in A[1]	Input	PIN_AD11	3A	B3A_N0	2.5 V (default)		12mA (default)	
in A[0]	Input	PIN_AF10	3A	B3A_N0	2.5 V (default)		12mA (default)	
in B[2]	Input	PIN_AF9	3A	B3A_N0	2.5 V (default)		12mA (default)	
in B[1]	Input	PIN_AC12	3A	B3A_N0	2.5 V (default)		12mA (default)	
in B[0]	Input	PIN_AB12	3A	B3A_N0	2.5 V (default)		12mA (default)	
in SEL[3]	Input	PIN_AE12	3A	B3A_N0	2.5 V (default)		12mA (default)	
in SEL[2]	Input	PIN_AD10	3A	B3A_N0	2.5 V (default)		12mA (default)	
in SEL[1]	Input	PIN_AC9	3A	B3A_N0	2.5 V (default)		12mA (default)	
in SEL[0]	Input	PIN_AE11	3A	B3A_N0	2.5 V (default)		12mA (default)	
out Y[3]	Output	PIN_V18	4A	B4A_N0	2.5 V (default)		12mA (default)	1 (default)
out Y[2]	Output	PIN_V17	4A	B4A_N0	2.5 V (default)		12mA (default)	1 (default)
out Y[1]	Output	PIN_W16	4A	B4A_N0	2.5 V (default)		12mA (default)	1 (default)
out Y[0]	Output	PIN_V16	4A	B4A_N0	2.5 V (default)		12mA (default)	1 (default)
out Y_LED[6]	Output	PIN_AH28	5A	B5A_N0	2.5 V (default)		12mA (default)	1 (default)
out Y_LED[5]	Output	PIN_AG28	5A	B5A_N0	2.5 V (default)		12mA (default)	1 (default)
out Y_LED[4]	Output	PIN_AF28	5A	B5A_N0	2.5 V (default)		12mA (default)	1 (default)
out Y_LED[3]	Output	PIN_AG27	5A	B5A_N0	2.5 V (default)		12mA (default)	1 (default)
out Y_LED[2]	Output	PIN_AE28	5A	B5A_N0	2.5 V (default)		12mA (default)	1 (default)
out Y_LED[1]	Output	PIN_AE27	5A	B5A_N0	2.5 V (default)		12mA (default)	1 (default)
out Y_LED[0]	Output	PIN_AE26	5A	B5A_N0	2.5 V (default)		12mA (default)	1 (default)

I have assigned my pins as such, "SW9-SW8-SW7-SW6" select the operation, "SW5-SW4- SW3" inputs A, "SW2-SW1-SW0" inputs B. "LED3- LED2- LED1- LED0 " outputs Y, " HEX6- HEX5- HEX4- HEX3- HEX2- HEX1- HEX0" outputs Y_LED for seven segment display.

Question 2)

Write a VHDL code that implements a BCD counter.

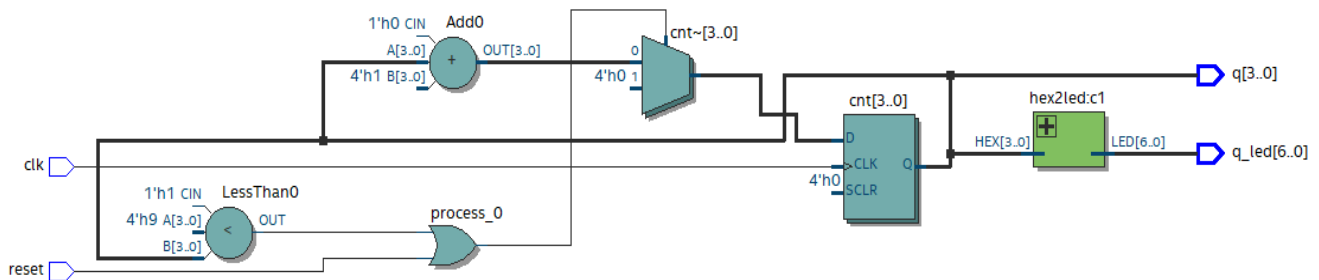


Figure5 - RTL schematic of BCD counter

VHDL Implementation of BCD Counter

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;

entity BCD_Counter is
    generic
    (
        MIN_COUNT : natural := 0;
        MAX_COUNT : natural := 9;
    )
    port
    (
        clk      : in std_logic;
        reset    : in std_logic;
        q        : out integer range MIN_COUNT to MAX_COUNT;
        q_led    : out std_logic_vector (6 DOWNTO 0));
end entity;

architecture rtl of BCD_Counter is

    component hex2led IS
        PORT (
            HEX : IN STD_LOGIC_VECTOR (3 DOWNTO 0);
            LED : OUT STD_LOGIC_VECTOR (6 DOWNTO 0)
        );
    end component;

    END component;
```

Code7 - VHDL of BCD Counter

```
signal cnt : integer range MIN_COUNT to MAX_COUNT;
signal temp : std_logic_vector (3 downto 0);

begin
    temp <= std_logic_vector(to_unsigned(cnt, temp'length));
    c1: hex2led port map(HEX => temp, LED => q_led);

    process (clk)
    begin
        if (rising_edge(clk)) then

            if reset = '1' or cnt >= 9 then
                -- Reset the counter to 0
                cnt <= 0;
            else
                -- Increment the counter if counting is enabled
                cnt <= cnt + 1;
            end if;


        end if;

        -- Output the current count
        q <= cnt;
    end process;
end rtl;
```

Code8 - VHDL of BCD Counter



Simulation Results of BCD Counter

 

Simulation5- BCD Counter

Pin Planner of BCD Counter

Node Name	Direction	Location	I/O Bank	VREF Group	I/O Standard	Reserved	Current Strength	Slew Rate
in clk	Input	PIN_AA15	3B	B3B_N0	2.5 V (default)		12mA (default)	
out q[3]	Output	PIN_V18	4A	B4A_N0	2.5 V (default)		12mA (default)	1 (default)
out q[2]	Output	PIN_V17	4A	B4A_N0	2.5 V (default)		12mA (default)	1 (default)
out q[1]	Output	PIN_W16	4A	B4A_N0	2.5 V (default)		12mA (default)	1 (default)
out q[0]	Output	PIN_V16	4A	B4A_N0	2.5 V (default)		12mA (default)	1 (default)
out q_led[6]	Output	PIN_AH28	5A	B5A_N0	2.5 V (default)		12mA (default)	1 (default)
out q_led[5]	Output	PIN_AG28	5A	B5A_N0	2.5 V (default)		12mA (default)	1 (default)
out q_led[4]	Output	PIN_AF28	5A	B5A_N0	2.5 V (default)		12mA (default)	1 (default)
out q_led[3]	Output	PIN_AG27	5A	B5A_N0	2.5 V (default)		12mA (default)	1 (default)
out q_led[2]	Output	PIN_AE28	5A	B5A_N0	2.5 V (default)		12mA (default)	1 (default)
out q_led[1]	Output	PIN_AE27	5A	B5A_N0	2.5 V (default)		12mA (default)	1 (default)
out q_led[0]	Output	PIN_AE26	5A	B5A_N0	2.5 V (default)		12mA (default)	1 (default)
in reset	Input	PIN_AA14	3B	B3B_N0	2.5 V (default)		12mA (default)	

Question 3)

Write a VHDL code that implements a sequence detector that detects the input "101". Overlaps must also be considered, that is, if a sequence of input "01010101100" occurs, then the output should remain logic high ("1") for three consecutive clock cycles.

 


Figure6 - RTL schematic of Sequence Detector

 


Figure7 – State Machine Viewer of Sequence Detector



```
library ieee;
use ieee.std_logic_1164.all;

entity sequence_detector is

    port(
        clk          : in    std_logic;
        input         : in    std_logic;
        reset         : in    std_logic;
        output        : out   std_logic
    );

end entity;

architecture rtl of sequence_detector is

    -- Build an enumerated type for the state machine
    type state_type is (s0, s1, s2, s3, s4);

    -- Register to hold the current state
    signal state : state_type;

begin

    -- Logic to advance to the next state
    process (clk, reset)
    begin

        if reset = '1' then
            state <= s0;

        elsif (rising_edge(clk)) then
            case state is
                when s0=>
                    if input = '1' then
                        state <= s1;
                    else
                        state <= s0;
                    end if;
            end case;
        end if;
    end process;
end architecture;
```


Code9 - VHDL of Sequence Detector

```
        when s1=>
            if input = '1' then
                state <= s1;
            else
                state <= s2;
            end if;
        when s2=>
            if input = '1' then
                state <= s3;
            else
                state <= s0;
            end if;
        when s3=>
            if input = '1' then
                state <= s1;
            else
                state <= s4;
            end if;
        when s4=>
            if input = '1' then
                state <= s3;
            else
                state <= s0;
            end if;
    end case;
end if;
end process;

-- Output depends solely on the current state
process (state)
begin
    case state is
        when s0=>
            output <= '0';
        when s1=>
            output <= '0';
        when s2=>
            output <= '0';
        when s3=>
            output <= '1';
        when s4=>
            output <= '1';
    end case;
end process;
end rtl;
```

Code10 - VHDL of Sequence Detector

Simulation Results of Sequence Detector

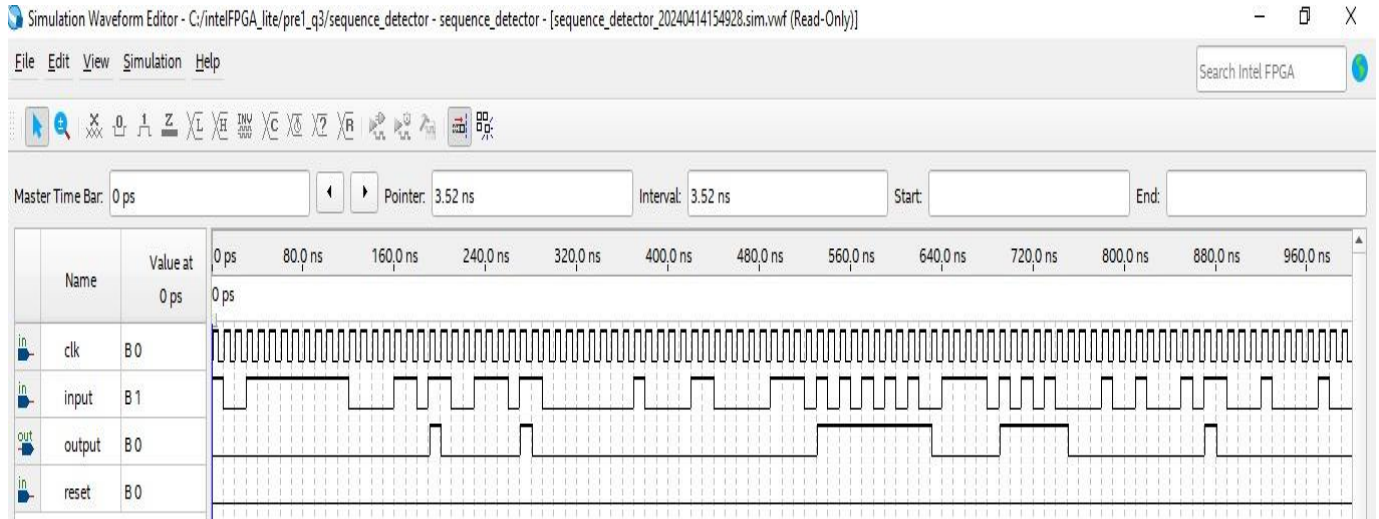

Simulation6- Sequence Detector

Pin Planner of Sequence Detector Design

Node Name	Direction	Location	I/O Bank	VREF Group	I/O Standard	Reserved	Current Strength	Slew Rate
in clk	Input	PIN_AA15	3B	B3B_N0	2.5 V (default)		12mA (default)	
in input	Input	PIN_AA14	3B	B3B_N0	2.5 V (default)		12mA (default)	
out output	Output	PIN_V16	4A	B4A_N0	2.5 V (default)		12mA (default)	1 (default)
in reset	Input	PIN_W15	3B	B3B_N0	2.5 V (default)		12mA (default)	

Comment: I have assigned my pins as such, "KEY0" for input, "KEY1" for clock, and "Key2" for reset. Have written my code with respect to the rising edge of the clock. Since my clock is linked to the "KEY1" when I release the button It will check the input and go to the related state.